
CMPEN 411

VLSI Digital Circuits

Spring 2012

Lecture 20: Multiplier Design

[Adapted from Rabaey's *Digital Integrated Circuits*, Second Edition, ©2003
J. Rabaey, A. Chandrakasan, B. Nikolic]

Review: Basic Building Blocks

❑ Datapath

- Execution units
 - Adder, multiplier, divider, shifter, etc.
- Register file and pipeline registers
- Multiplexers, decoders

❑ Control

- Finite state machines (PLA, ROM, random logic)

❑ Interconnect

- Switches, arbiters, buses

❑ Memory

- Caches (SRAMs), TLBs, DRAMs, buffers

Diagram illustrating the long multiplication process for the binary numbers 10101010 (Multiplicand) and 1011 (Multiplier).

The multiplicand is 10101010 and the multiplier is 1011. The partial products are shown, with the multiplier bit 1 highlighted in the third position (from the right).


The partial products are:

- 10101010
- 10101010
- 00000000
- 10101010

The final result is 11100110.

Multiply Operation

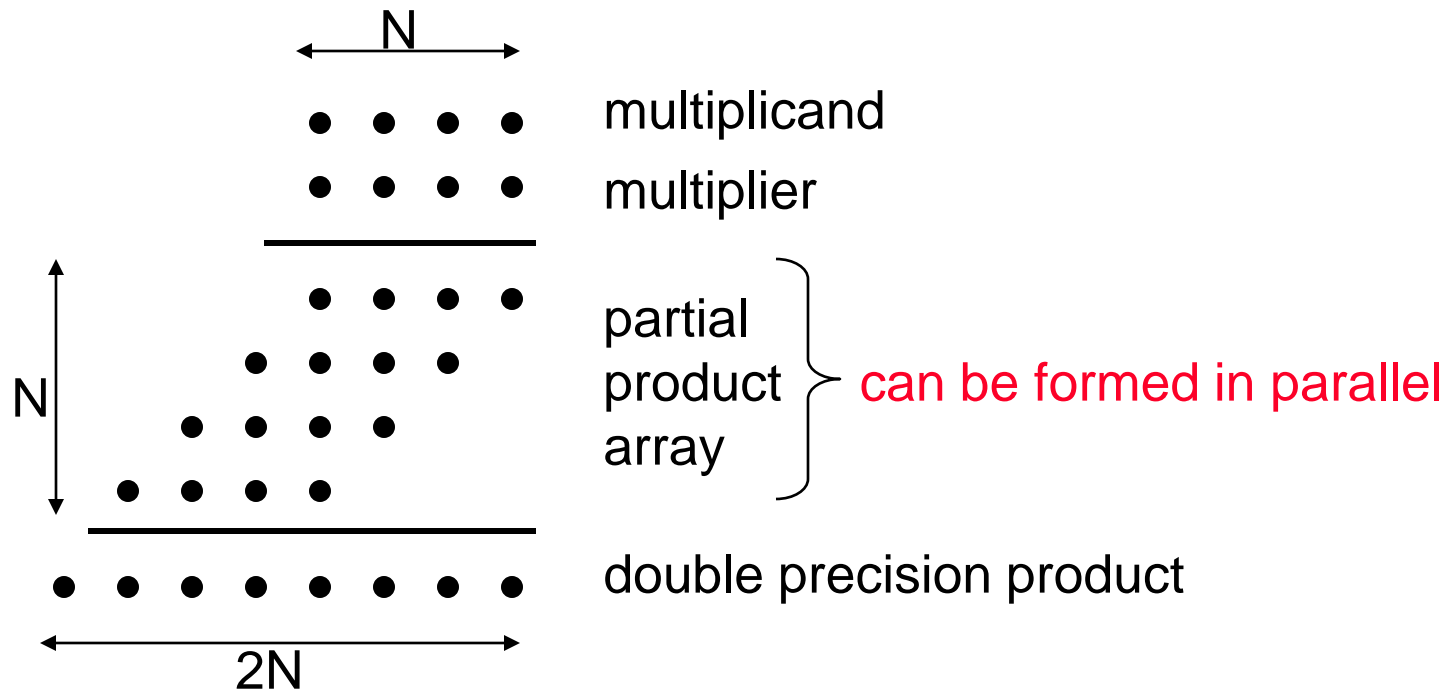- ❑ Multiplication is just a a lot of additions



Multiplication Approaches

❑ Right shift and add

- Partial product array rows are accumulated from top to bottom on an N-bit adder
 - After each addition, right shift (by one bit) the accumulated partial product to align it with the next row to add
- Time for N bits $T_{\text{serial_mult}} = O(N T_{\text{adder}}) = O(N^2)$ for a RCA


❑ Making it faster

- Use a faster adder
- Use higher radix (e.g., base 4) multiplication – $O(N/2 T_{\text{adder}})$
 - Use **multiplier recoding** to simplify multiple formation (booth)
- Form the partial product array in parallel and add it in parallel


❑ Making it smaller (i.e., slower)

- Use serial-parallel mult
- Use an array multiplier
 - Very regular structure with only short wires to nearest neighbor cells. Thus, very simple and efficient layout in VLSI Can be easily and efficiently pipelined

Serial-parallel multiplier structure

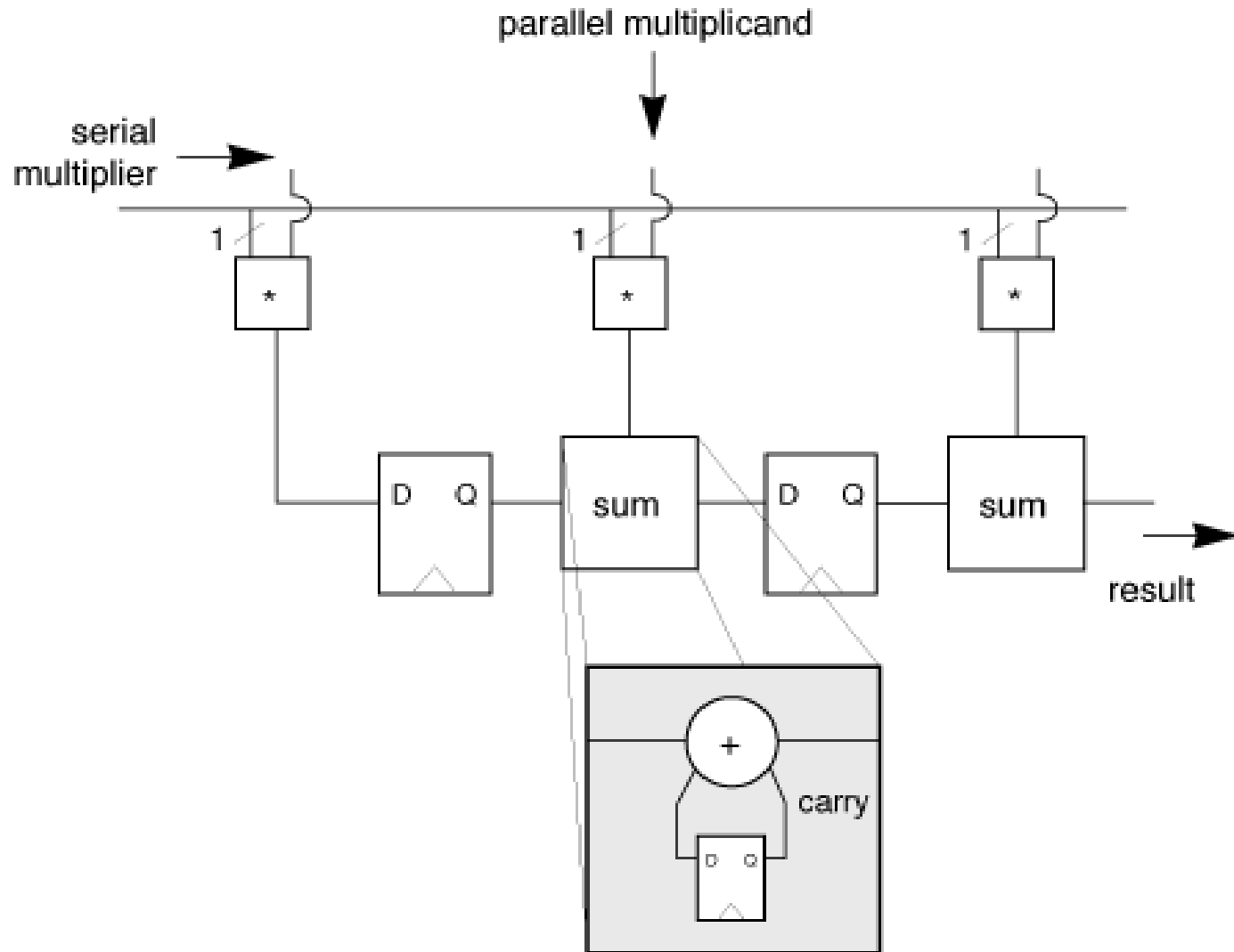

The Array Multiplier

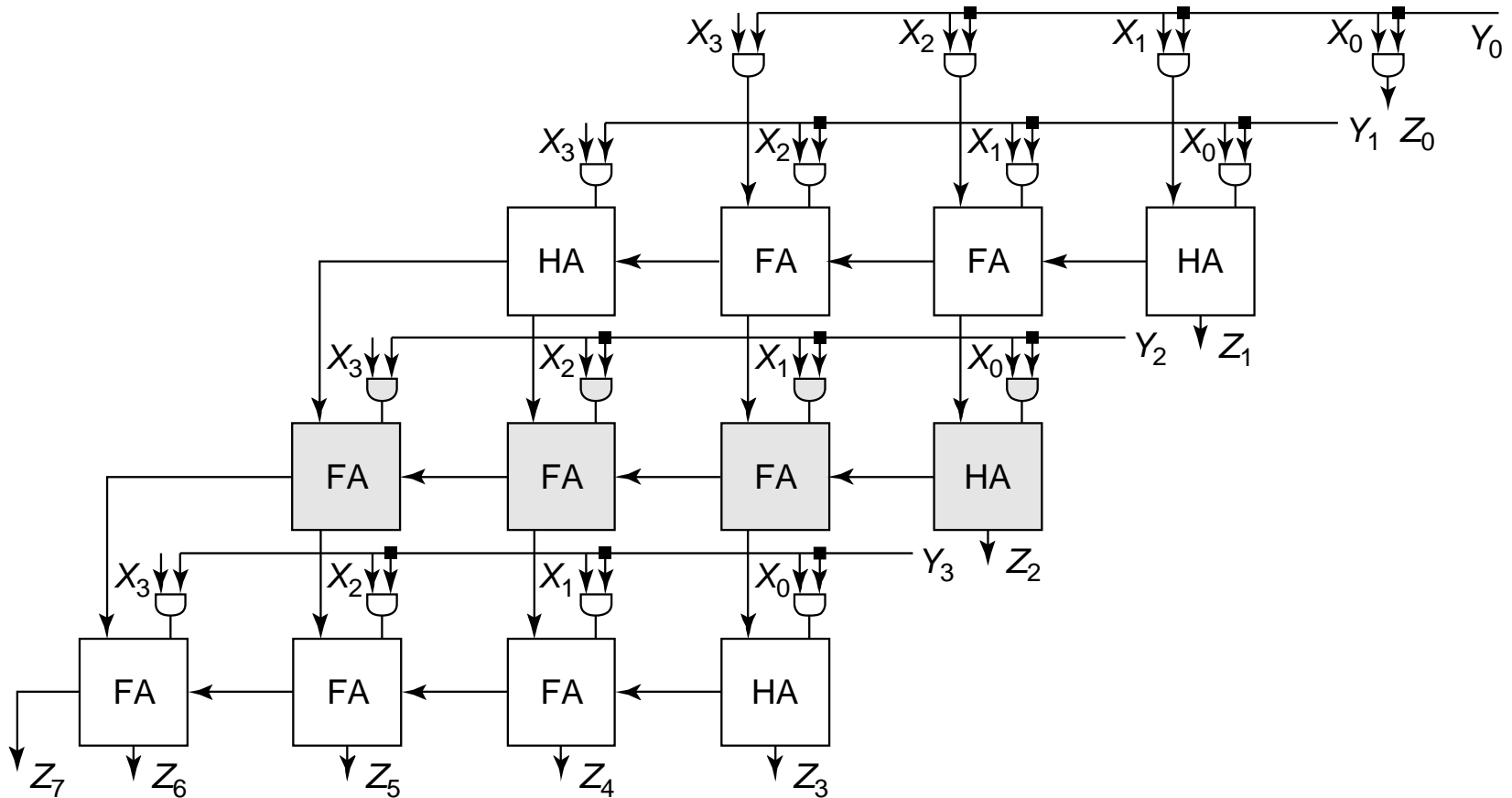

Booth multiplier

- ❑ Encoding scheme to reduce number of stages in multiplication.
- ❑ Performs two bits of multiplication at once—requires half the stages.
- ❑ Each stage is slightly more complex than simple multiplier, but adder/subtractor is almost as small/fast as adder.

Booth encoding

- ❑ Two's-complement form of multiplier:
 - $y = -2^n y_n + 2^{n-1} y_{n-1} + 2^{n-2} y_{n-2} + \dots$ (first bit is the sign bit)
(example, $y=18=010010$ $y=-18=101110$)
- ❑ Rewrite using $2^a = 2^{a+1} - 2^a$:
 - $y = 2^n(y_{n-1}-y_n) + 2^{n-1}(y_{n-2}-y_{n-1}) + 2^{n-2}(y_{n-3}-y_{n-2}) + \dots$
- ❑ Consider first two terms: by looking at three bits of y , we can determine whether to add x , $2x$ to partial product.

Booth actions

- $y = 2^n(y_{n-1}-y_n) + 2^{n-1}(y_{n-2}-y_{n-1}) + 2^{n-2}(y_{n-3}-y_{n-2}) + \dots$

- Consider first two terms: by looking at three bits of y , we can determine whether to add x , $2x$ to partial product.


y_i	y_{i-1}	y_{i-2}	increment
0	0	0	0
0	0	1	x
0	1	0	x
0	1	1	$2x$
1	0	0	$-2x$
1	0	1	$-x$
1	1	0	$-x$
1	1	1	0

Booth example


- ❑ $x = 1001$ (9_{10}), $y = 0111$ (7_{10}).
- ❑ $P_0 = 00000000$
- ❑ $y_3y_2y_1=011$ $y_1y_0y_{-1}=11(0)$
- ❑ $y_1y_0y_{-1} = 110$, $P_1 = P_0 - (1001) = 11110111$
- ❑ x shift left for 2 bits to be 100100
- ❑ $y_3y_2y_1 = 011$, $P_2 = P_1 + (10*100100) =$
 $11110111 + 01001000 = 001111111$ (63_{10})
- ❑ An array multiplier needs N additions, booth multiplier needs only $N/2$ additions

Review: A 64-bit Adder/Subtractor

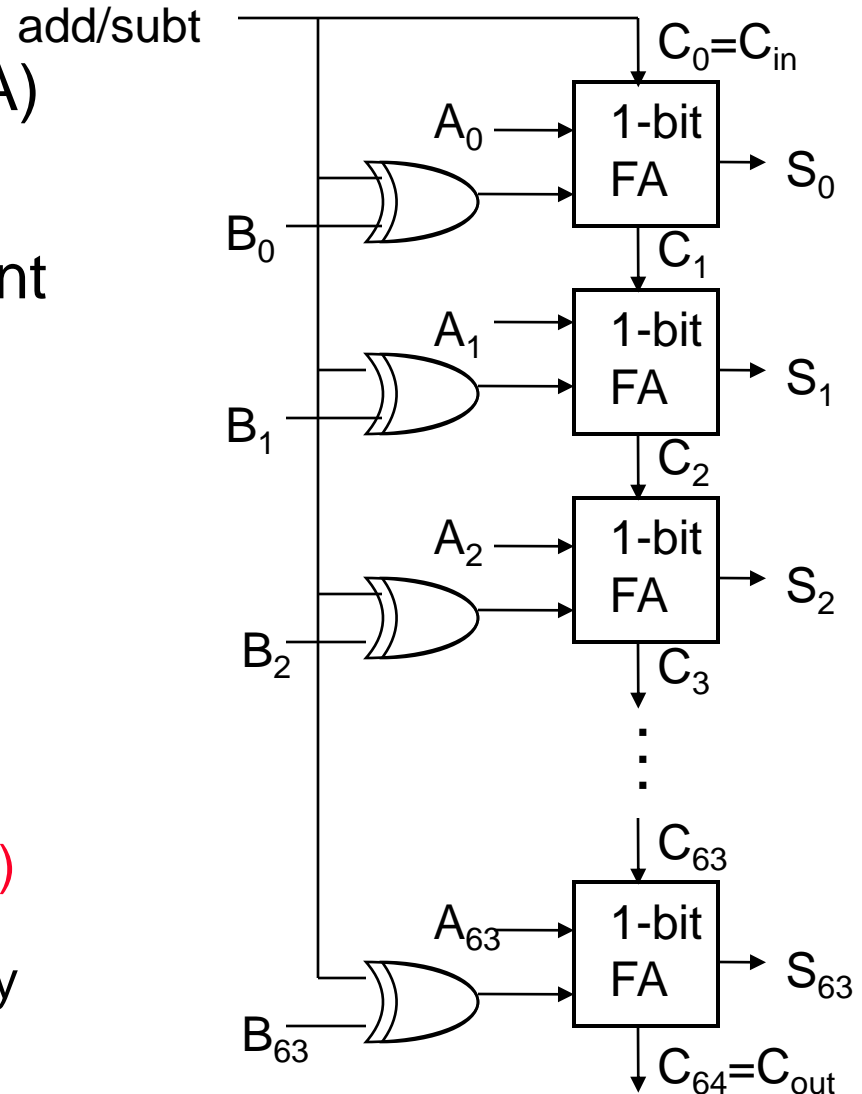- ❑ Ripple Carry Adder (RCA)
built out of 64 FAs
- ❑ Subtraction – complement
all subtrahend bits (xor
gates) and set the low
order carry-in
- ❑ RCA
 - advantage: simple logic,
so small (low cost)
 - disadvantage: slow ($O(N)$
for N bits) and lots of
glitching (so lots of energy
consumption)




Booth structure

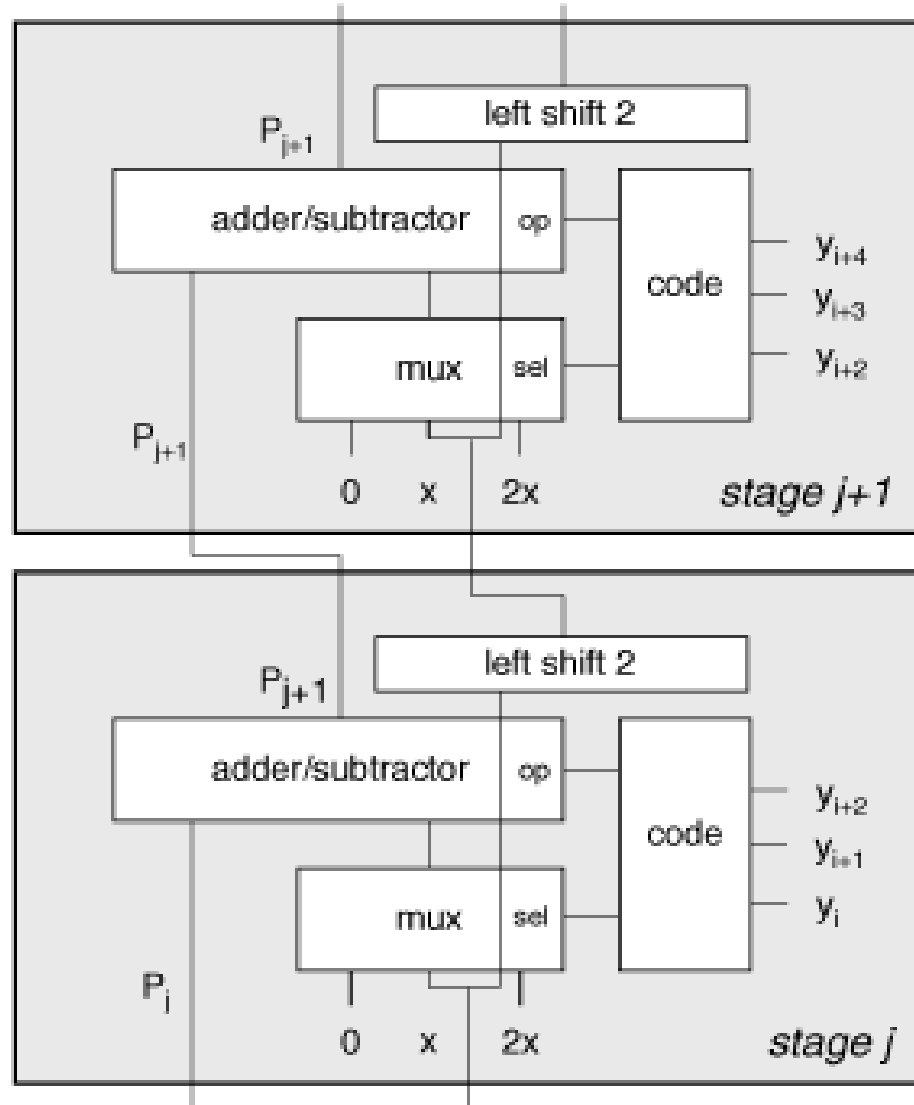


Wallace-Tree Multiplier

Partial products

 


(a)

First stage

 


(b)

Second stage

 


(c)

Final adder

 


(d)

Wallace-Tree Multiplier

 


Full adder = (3,2) compressor

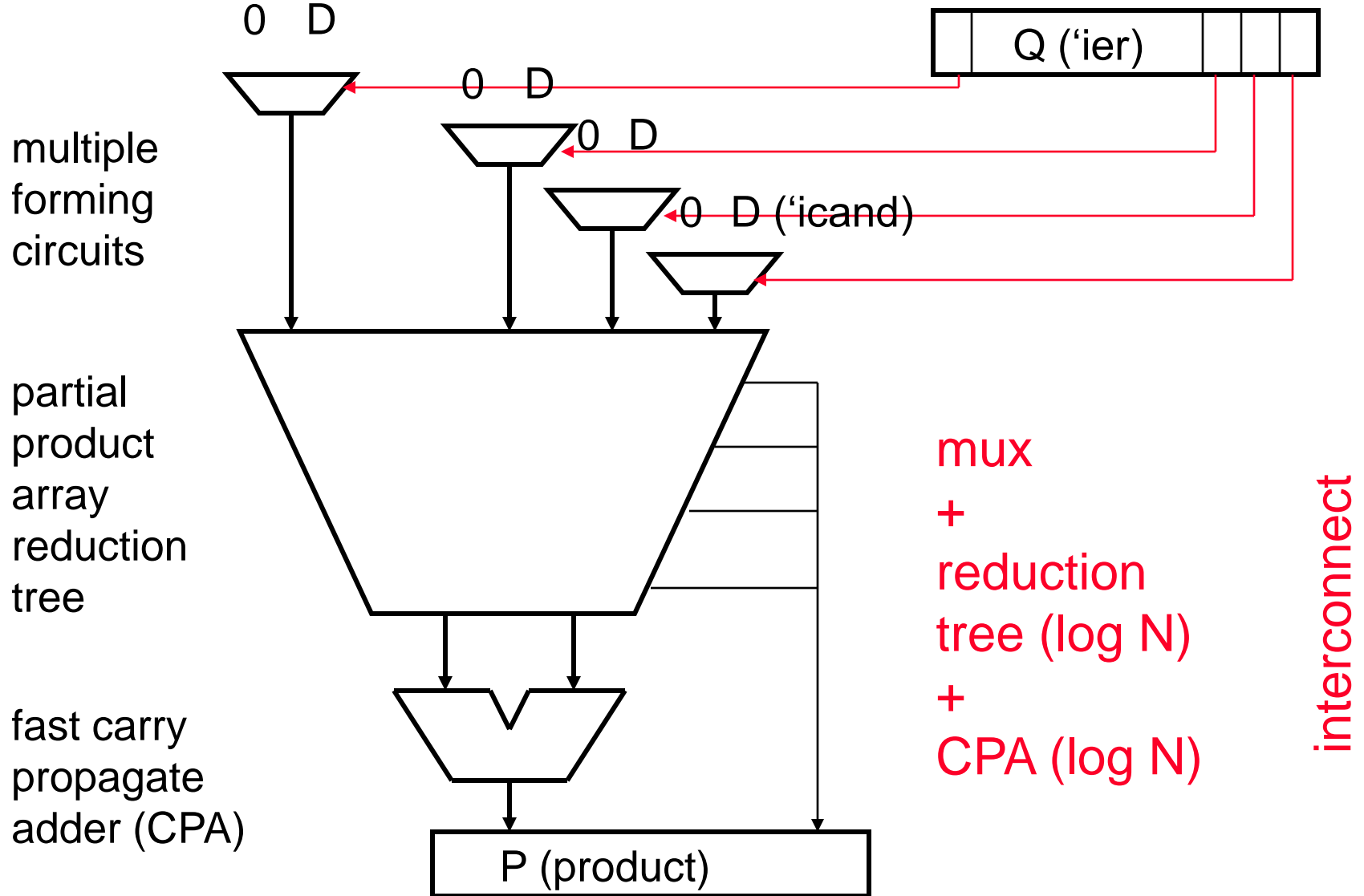
Making it Faster: Tree Multiplier Structure



(4,2) Counter

 


 - ❑ Built out of two (3,2) counters (just FA's!)
 - all of the inputs (4 external plus one internal) have the **same weight** (i.e., are in the **same** bit position)
 - the **internal** carry output is fed to the next higher weight position (indicated by the \leftarrow)



Note: Two carry outs - one “**internal**” and one “**external**”

Tiling (4,2) Counters


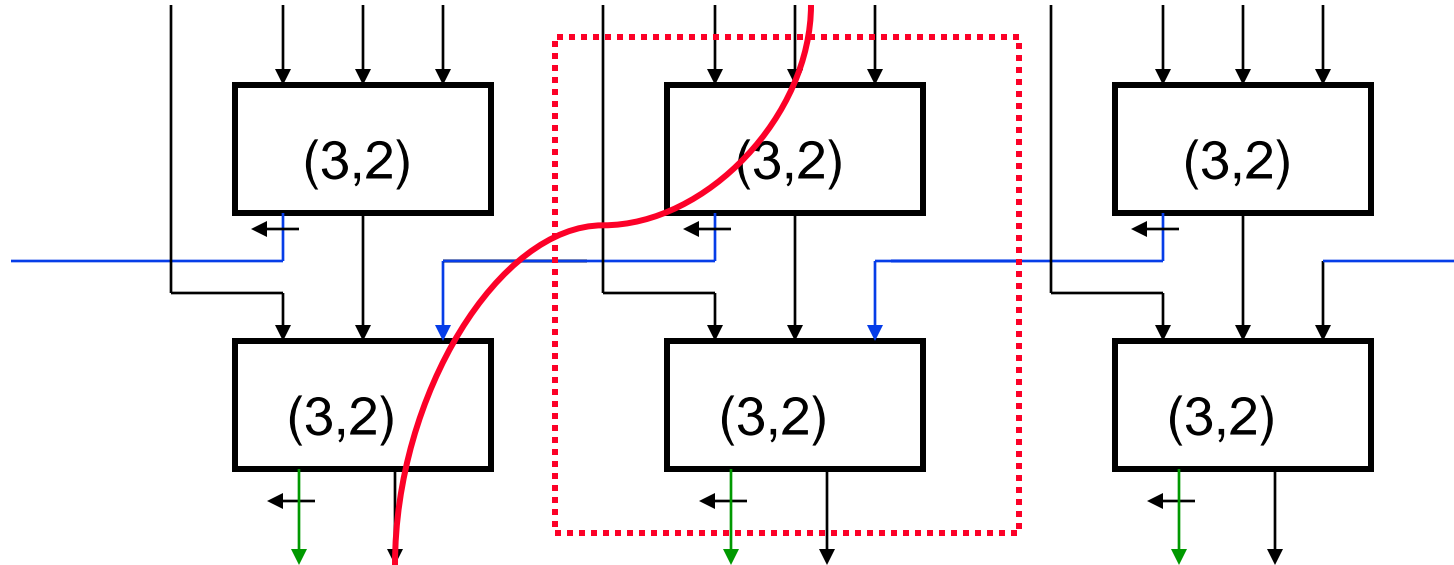


- ❑ Reduces columns **four** high to columns only **two** high
 - Tiles with neighboring (4,2) counters
 - **Internal** carry in at same “level” (i.e., bit position weight) as the **internal** carry out

4x4 Partial Product Array Reduction


Fast 4x4 multiplication using (4,2) counters

How would you lay it out?

  


8x8 Partial Product Array Reduction

❑ Wallace tree multiplier

 

An 8x8 Multiplier Layout

- How should it be laid out?

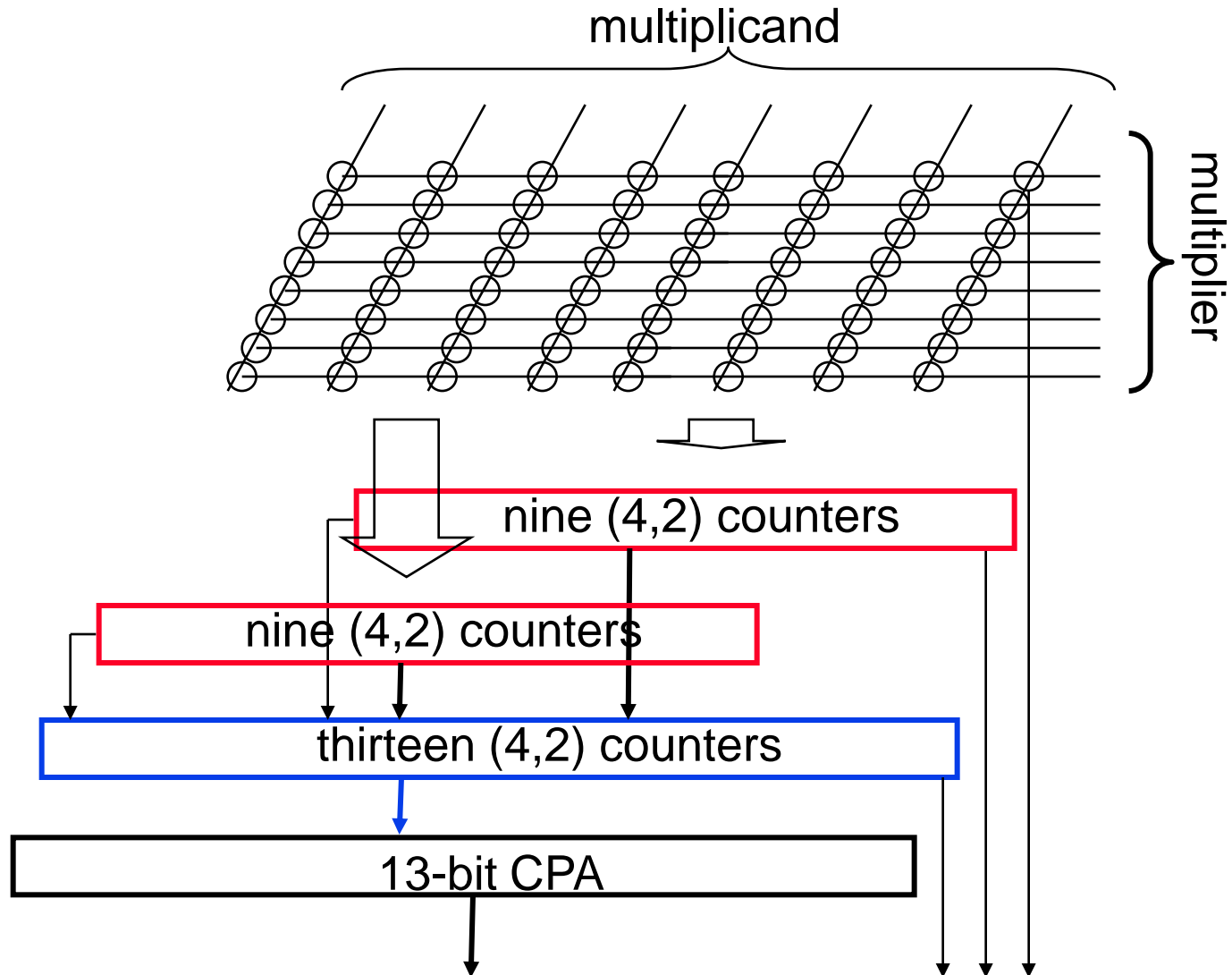

Multipliers —Summary

- **Optimization Goals Different Vs Binary Adder**
- **Once Again: Identify Critical Path**
- **Other possible techniques**
 - **Logarithmic versus Linear (Wallace Tree Mult)**
 - **Data encoding (Booth)**
 - **Pipelining**

FIRST GLIMPSE AT SYSTEM LEVEL OPTIMIZATION

Next Lecture and Reminders

□ Next lecture

- Shifters, decoders, and multiplexers
 - Reading assignment – Rabaey, et al, 11.5-11.6